
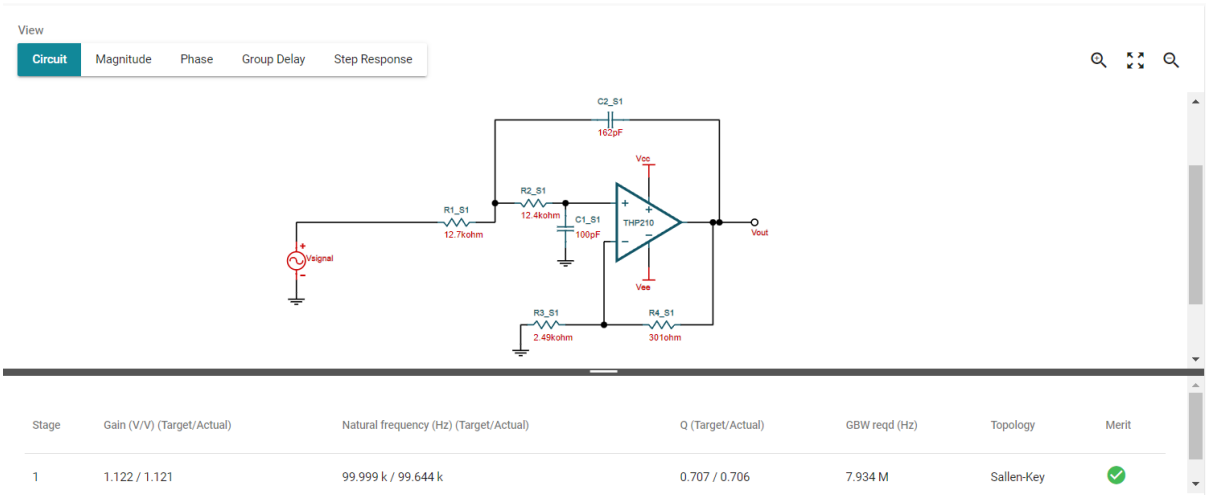



1. webench Circuit Diagram

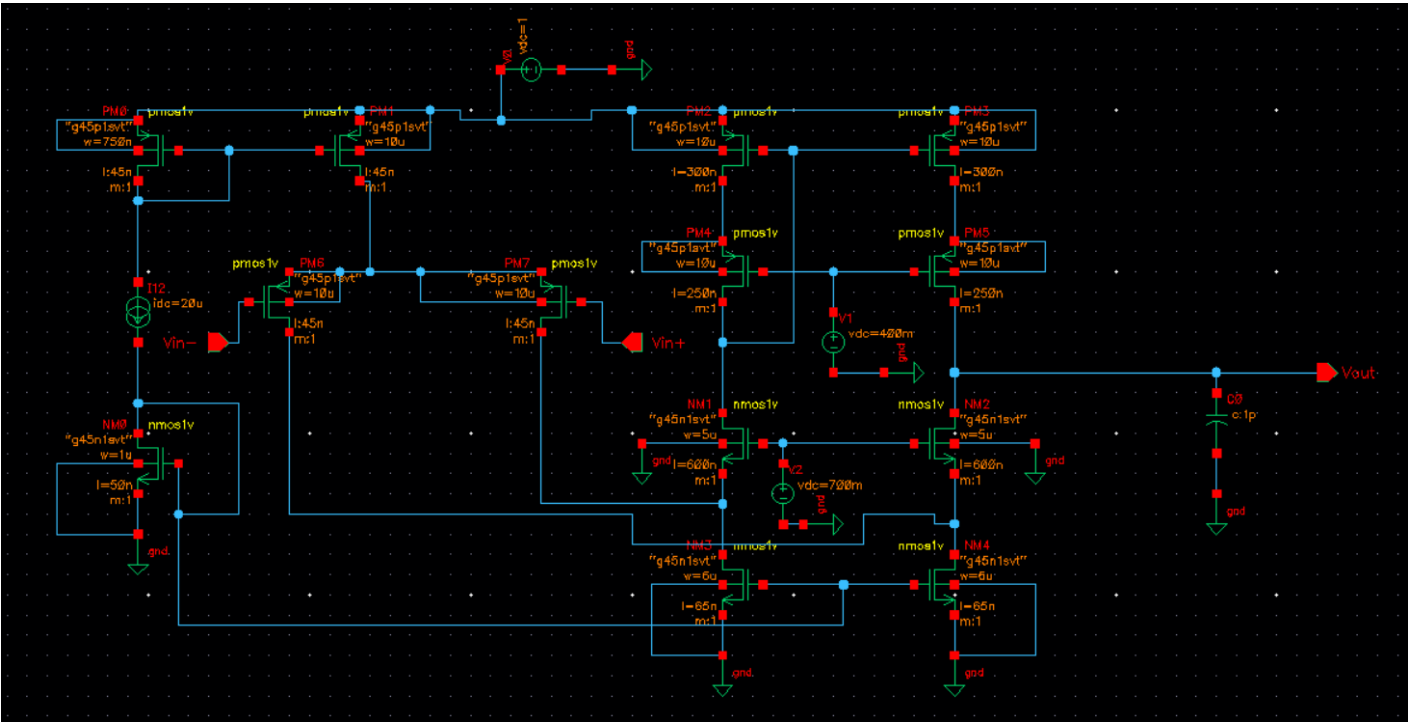

2. Transistor Sizings




3. DC Operating Points

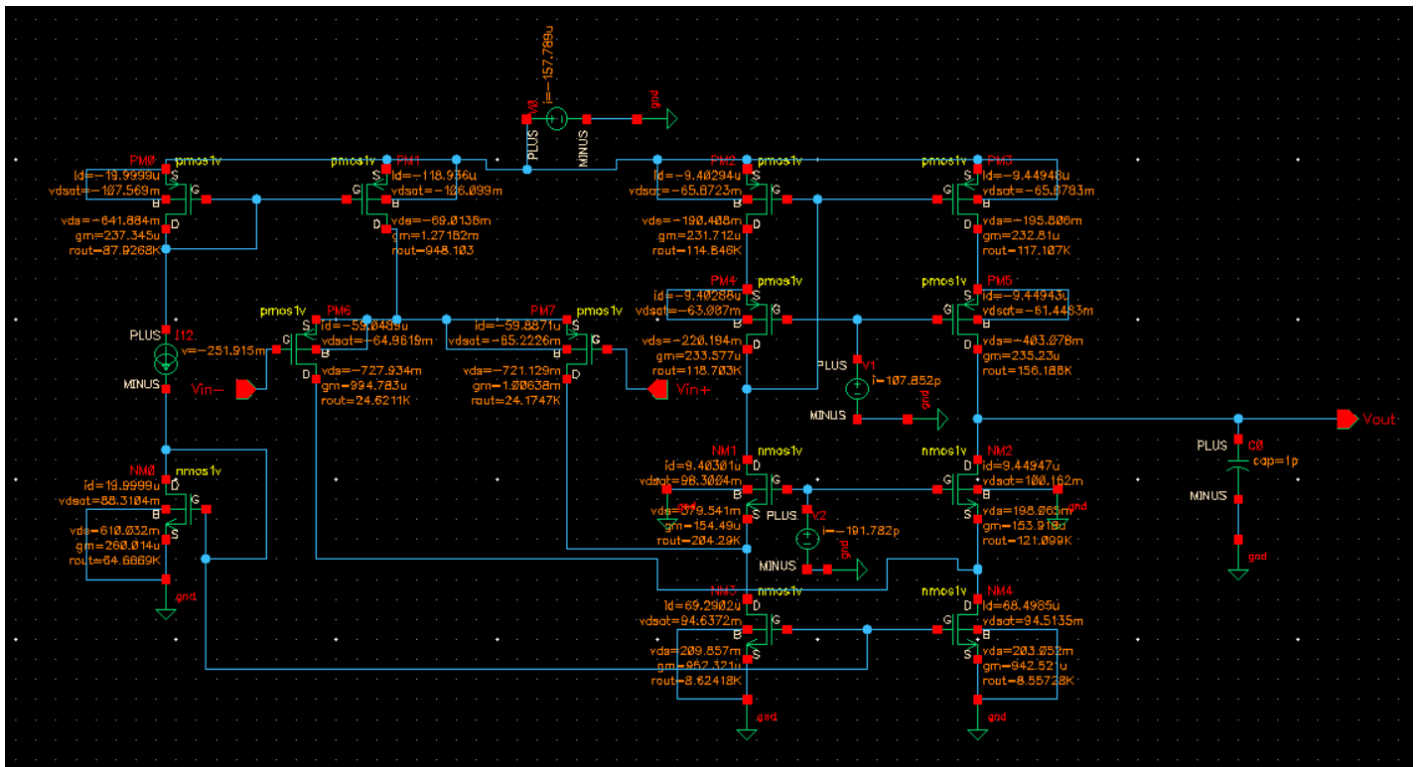


4. Op-amp STB analysis

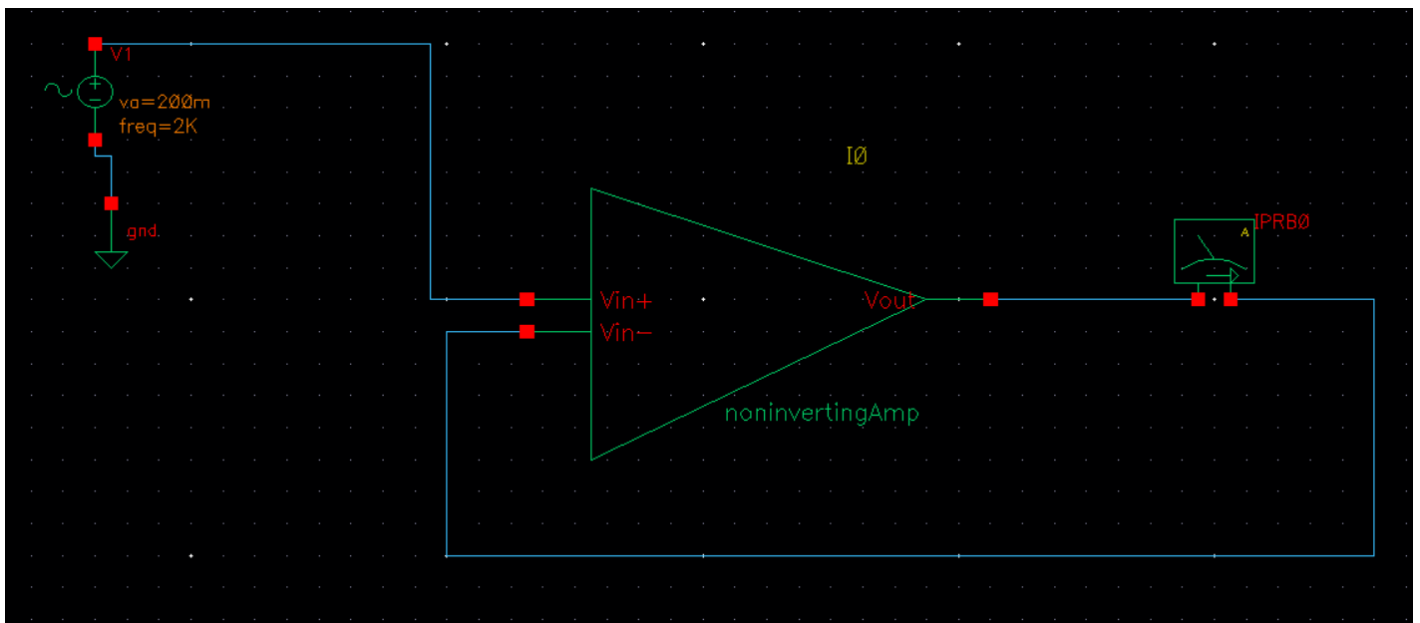
4.1 - Setting up Unity Gain configuration




4.2 - Process Corner results (Summary)

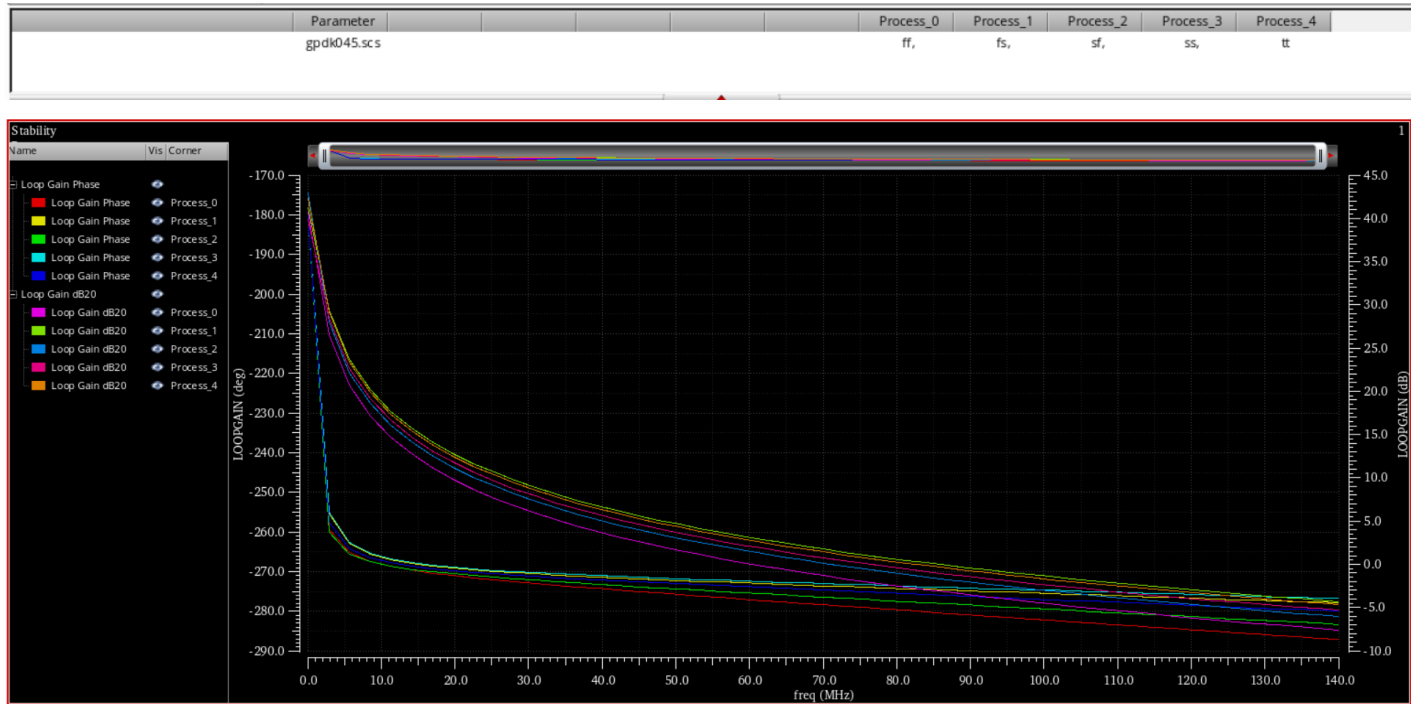


4.3 - ff corner

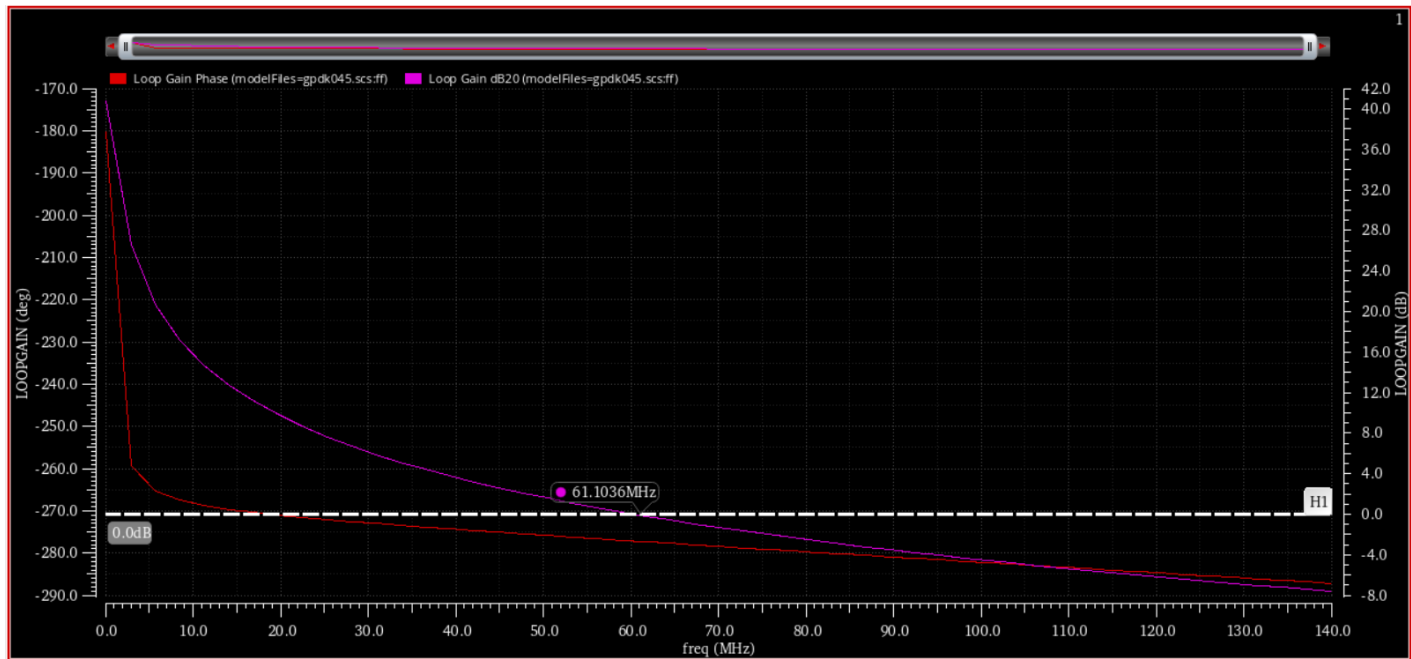


4.4 - fs corner

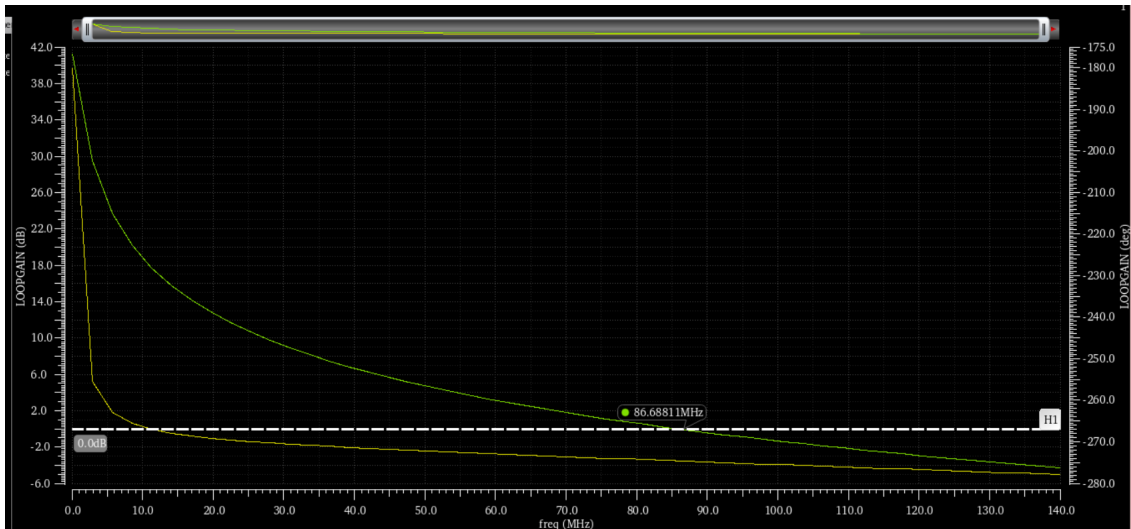


4.5 - sf corner

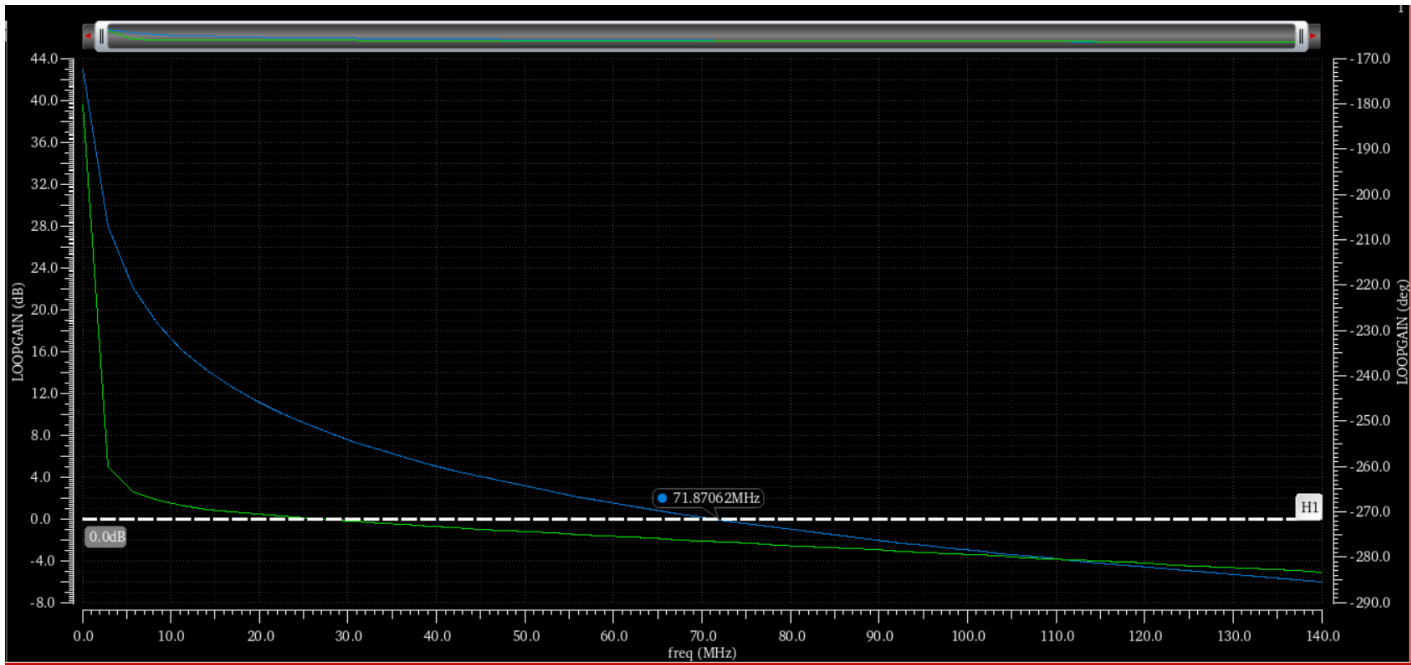

4.6 - ss corner

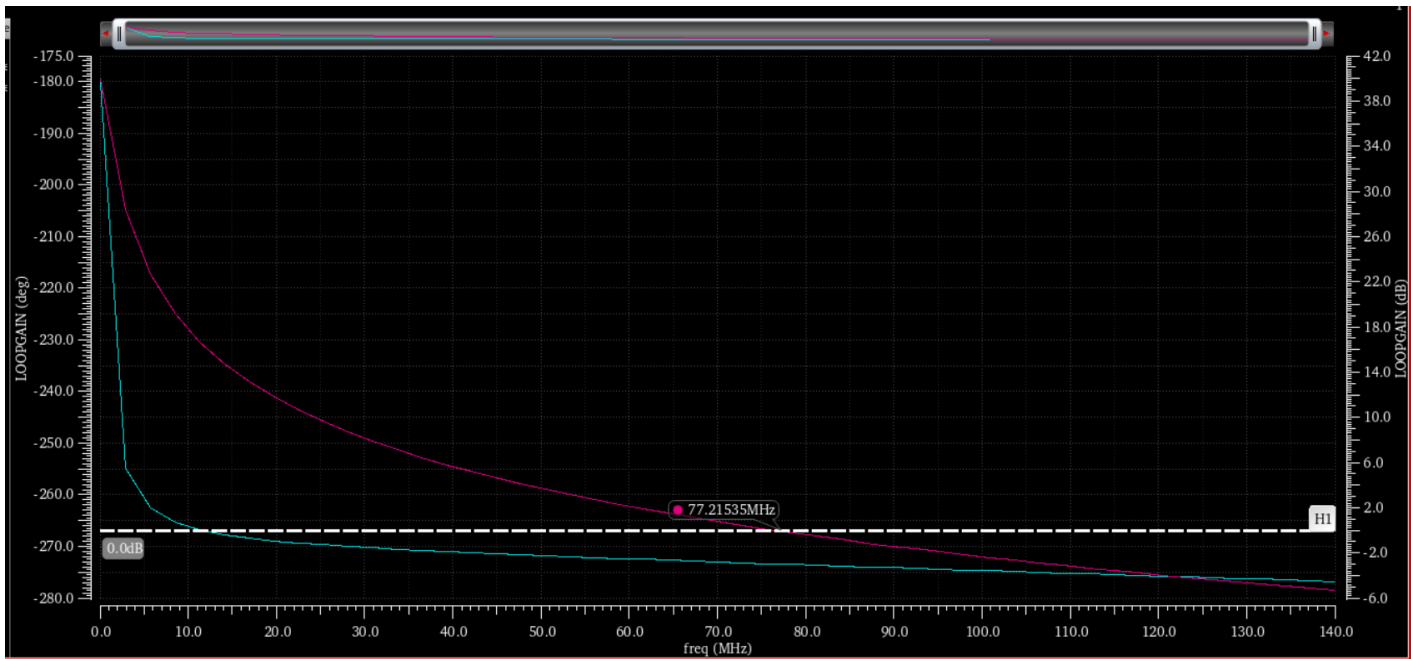

4.7 - tt corner

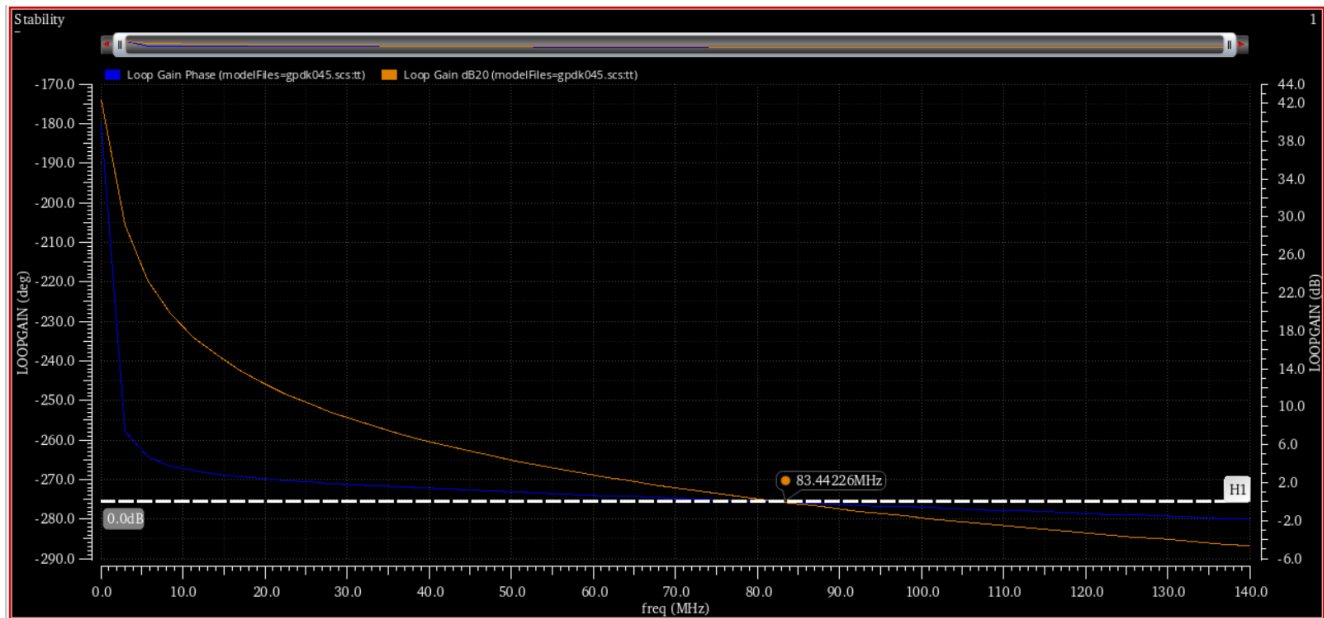

5. Magnitude response of Butterworth Filter

